

# Chapter 18

## Combinational Behavioral SystemVerilog

ECEn 220

### Fundamentals of Digital Systems



# Behavioral Design

- Used for creating both combinational and sequential circuits
  - Combinational: output depends only on inputs
  - Sequential: output depends on inputs and state
- Behavioral SystemVerilog syntax for creating logic is critical - you must learn the syntax style
  - It is possible to accidentally create sequential circuits when you want combinational circuits
  - It is possible to create code that is "non-synthesizable"
  - It is easy to make mistakes!

# always\_comb Blocks

- Combinational logic can be created using always\_comb blocks
  - This declares your intent to the synthesizer that you **only want combinational logic**
  - Throws an error if you unintentionally create sequential circuits
- Can contain case statements, if-then-else statements, etc. **(Not available for structural and Dataflow)**
- Same operators used in Dataflow are available in always\_comb blocks
- Uses the blocking assignment statement
- **Considered part of behavioral SystemVerilog**

# Blocking vs. Non-Blocking

## Blocking

- Only used in `always_comb` blocks
- `<variable> = <statement>`
- Statements are executed sequentially, similar to C-code.
- Used for combinational logic

## Non-blocking

- Only used in `always_ff` blocks
- `<variable> <=> <statement>`
- Statements are executed in parallel.
- Used for sequential logic

**Do not mix blocking and non-blocking assignments in one always block**

# Blocking vs. Non-Blocking

## Blocking

```
always_comb
Begin
    B = ~A;
    C = B & A;
    D = C & A;
end
```

### When a signal changes:

B gets A's value, then  
C gets B's new value, and then  
D gets C's new value.

This always block puts A's value into  
B, C, and D.

Assignments must be in the right order.


Structural Design — Built-in gates

Dataflow — operators, cond. ..

Behavioral Design —

**always\_comb**

**always\_ff**

 

```
Module XYZ (...);
```

```
assign A = W&X;
```

```
assign A = (W > 0) ? 1'b1 : 1'b0;
```

```
always_comb
```

```
Begin
```

```
    B = ~A;
```

```
    C = B & A;
```

```
    D = C & A;
```

```
End
```

```
endmodule
```

# Blocking vs. Non-Blocking


## Non-Blocking

```
always_ff @(posedge clk)
begin
    B <= A;
    C <= B;
    D <= C;
end
```

On every clock edge:

B gets A's value,  
C gets B's **old** value, and  
D gets C's **old** value.

 Order of assignments **DOES NOT MATTER...**



Individual statement semantics are sequential. Should be **coded in order of logic flow**.

```
always_comb begin
  b = a;
  c = b;          // c = a
end
```

**Not intended.**

```
always_comb begin
  c = b;          // c = previous value of a
  b = a;          // changing b does not re-trigger the always_comb in this
                  // time step
end
```

# 'if' Statement

## Syntax

```
if (expression)  
begin  
    ...statements...  
end
```

```
else if (expression)  
begin  
    ...statements...  
end  
    ...more else if blocks
```

```
else  
begin  
    ...statements...  
end
```


Note: "Begin" and "end" keywords  
(used if more than one statement in clause)

Example:

```
if (alu_func == 2'b00)  
    aluout = a + b;  
else if (alu_func == 2'b01)  
    aluout = a - b;  
else if (alu_func == 2'b10)  
    aluout = a & b;  
else // alu_func == 2'b11  
    aluout = a | b;
```



# If Statement Examples

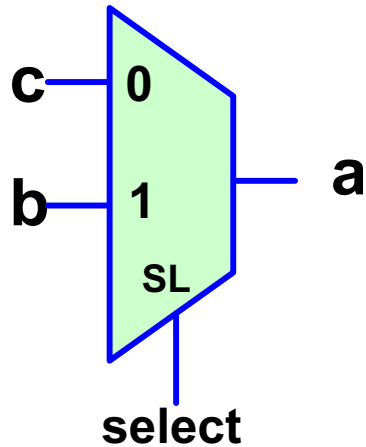

```
always_comb begin
    if(select) a=b;
    else      a=c;
end
```

```
// Nested IF
statements
always_comb begin
    if(large == 1'b1)
        if (e>f)
            a=e;
        else
            a=f;
    else
        if (e<f)
            a=e;
        else
            a=f;
end
```

```
// Decoder
always_comb begin
    if(s==2'b00)
        a=4'b0001;
    else if(s==2'b01)
        a=4'b0010;
    else if(s==2'b10)
        a=4'b0100;
    else
        a=4'b1000;
end
```

```
// Multiple
assignments
always_comb begin
    if(select) begin
        a=b;
        z=x;
    end
    else begin
        a=c;
        z=y;
    end
end
```

# Covering All Cases

- For combinational logic, you must **cover all cases** when using an if statement
  - Otherwise a “latch” will be inferred

```
// Bad Example #1
always_comb begin
    if (s==2'b00)
        a=4'b0001;
    else if (s==2'b01)
        a=4'b0010;
    else if (s==2'b10)
        a=4'b0100;
end
```

```
// Bad Example #2
always_comb begin
    if (a<b)
        w=2'b01;
    else if (a>b)
        x=2'b10;
    else
        y=2'b11;
end
```

What happens when  $s==2'b11$ ?

The synthesis tool needs to “remember” what a used to be. Infers a latch for a – not combinational)

What is wrong with this?

w, x, and y are not **all** assigned values **under all conditions**. Infers latches for w, x, and y.

# Covering All Cases

```
// Bad Example #1
always_comb begin
    if(s==2'b00)
        a=4'b0001;
    else if(s==2'b01)
        a=4'b0010;
    else if(s==2'b10)
        a=4'b0100;
    else
        a=4'b0000;
end
```

Always include an “else” statement.  
Or a='X; to indicate something is wrong such as s is 'X' in simulation.

```
// Bad Example #2
always_comb begin
    w=2'b00;
    x=2'b00;
    y=2'b00;
    if(a<b)
        w=2'b01;
    else if(a>b)
        x=2'b10;
    else
        y=2'b11;
end
```

Assign default values to all signals.

# case statements

## Syntax

```
case (expression)
  case_choice1:
  begin
    ...statements...
  end
```

```
case_choice2:
  begin
    ...statements...
  end
```

...more case choices blocks...

```
default:
  begin
    ...statements...
  end
endcase
```


Note: "Begin" and "end" keywords  
(used if more than one statement in clause)

Example:

```
case (alu_ctr)
  2'b00: aluout = a + b;
  2'b01: aluout = a - b;
  2'b10: aluout = a & b;
  default: aluout = 1'bx; // Treated as don't cares for
endcase // minimum logic generation.
```

Note: endcase keyword

# case statement examples

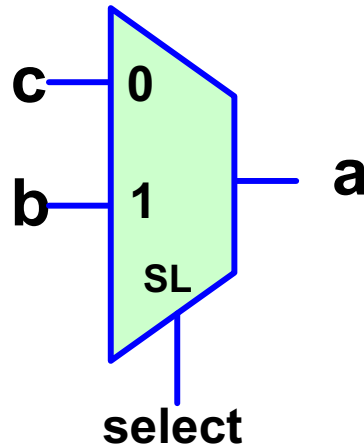

```
case (select)
  1'b1: a=b;
  1'b0: a=c;
endcase
```

```
// Decoder
always_comb begin
  case(select)
    2'b00: a=4'b0001;
    2'b01: a=4'b0010;
    2'b10: a=4'b0100;
    default: a=4'b1000;
  endcase
end
```

```
// Multiple assignments
always_comb begin
  case(select)
    2'b00: begin
      a=4'b0001;
      b=2'b01;
    end
    2'b01: begin
      a=4'b0101;
      b=2'b11;
    end
    2'b10: begin
      a=4'b1111;
      b=2'b00;
    end
    default: begin
      a=4'b0000;
      b=2'b10;
    end
  endcase
end
```

# Covering all cases

- Like the 'if' statement, you must cover all cases when using a case statement for combinational logic
  - Otherwise a "latch" will be inferred

```
// Bad #1
always_comb begin
    case(s)
        2'b00: a=4'b0001;
        2'b01: a=4'b0010;
        2'b10: a=4'b0100;
    endcase
end
```

## What happens when $s=2'b11$ or 'XX'?

The synthesis tool needs to "remember" what a used to be (infers a latch – not combinational)

```
// Bad #2
always_comb begin
    case(select)
        2'b00:
            a=4'b0001;
        2'b01:
            b=2'b11;
        2'b10:
            c=4'b1111;
        default:
            d=4'b0000;
    endcase
end
```

a, b, and c are not all assigned values under all conditions. Infers latches for a, b, and c.

# Covering all cases

```
// Bad #1
always_comb begin
  case(s)
    2'b00: a=4'b0001;
    2'b01: a=4'b0010;
    2'b10: a=4'b0100;
    default:
      a=4'b0000;
  endcase
end
```

Always include a 'default' statement.  
Or default: a='X'; to indicate  
something is wrong such as when s  
is 'X' in simulation.

Assign default values to all  
signals.

```
// Bad #2
always_comb begin
  a=4'b0000;
  b=4'b0000;
  c=4'b0000;
  d=4'b0000;
  case(select)
    2'b00:
      a=4'b0001;
    2'b01:
      b=2'b11;
    2'b10:
      c=4'b1111;
    default:
      d=4'b0000;
  endcase
end
```